Basic Formulas For Electrical Engineering

Basic Formulas for Electrical Engineering

Electrical engineering is built on a foundation of concise, powerful equations that translate physical phenomena into numbers we can manipulate. Whether you're a student tackling your first lab, a technician troubleshooting a circuit, or an experienced engineer designing a power plant, a solid grasp of the **basic formulas for electrical engineering** is indispensable. In this article, we'll walk through the most essential equations, explain their practical relevance, and give you quick tips for applying them in real-world scenarios.

1. Ohm's Law and Power Equations

Ohm's Law

The cornerstone of all circuit analysis, Ohm's Law links voltage (V), current (I), and resistance (R):

- **V = I × R**
- **I = V ÷ R**
- **R = V ÷ I**

These simple relationships let you calculate any one of the three variables when the other two are known.

Power in DC Circuits

Power (P) is the rate at which electrical energy is consumed or delivered. In direct current (DC) systems, power is expressed as:

- **P = V × I**
- **P = I² × R**
- **P = V² ÷ R**

Use the form that best matches the known quantities. For example, if you know the current and resistance, the **I² × R** expression is quickest.

2. AC Circuit Fundamentals

Phasor Representation

Alternating current (AC) adds a phase dimension. Voltages and currents are represented as phasors, complex numbers that encode magnitude and phase angle. The AC equivalents of Ohm's Law involve impedance (Z):

Downloaded from www.suitsbysuits.com by Elaina & Ellen • Explore the unseen. • Page 1 • 2026-06-28

- **$V = I \times Z$**
- **$I = V \div Z$**

Impedance of Basic Elements

Impedance extends resistance to AC circuits, incorporating reactance:

- **Resistor: $Z = R$**
- **Inductor: $Z = j\omega L$**
- **Ceramic Capacitor: $Z = 1 \div (j\omega C)$**

Here, **j** is the imaginary unit, **ω** is angular frequency (2πf), and **L** and **C** are inductance and capacitance, respectively.

3. Impedance and Reactance

Reactance Calculations

Reactance quantifies how inductors and capacitors oppose AC flow:

- **Inductive Reactance: $X_L = \omega L = 2\pi fL$**
- **Capacitive Reactance: $X_C = 1 \div (\omega C) = 1 \div (2\pi fC)$**

These values are added to resistance in the complex plane to form total impedance.

Magnitude of Impedance

The overall impedance magnitude is found via:

- **$|Z| = \sqrt{(R^2 + (X_L - X_C)^2)}$**

4. Transformers and Power Distribution

Turns Ratio

Transformers step voltage up or down while conserving power (ideal case). The turns ratio (n) is:

- **$n = V_{primary} \div V_{secondary} = N_{primary} \div N_{secondary}$**

Efficiency and Losses

Real transformers incur copper and iron losses. Efficiency (η) is approximated by:

- **$\eta = (P_{secondary} \div P_{primary}) \times 100\%$**

5. Circuit Analysis Techniques

Kirchhoff's Laws

Kirchhoff's Voltage Law (KVL) and Kirchhoff's Current Law (KCL) provide systematic methods for solving complex networks:

- **KVL:** $\Sigma V_{\text{around loop}} = 0$
- **KCL:** $\Sigma I_{\text{entering node}} = \Sigma I_{\text{leaving node}}$

Node Voltage Method

Choose a reference ground node, write KCL equations for each remaining node, and solve the resulting linear system. This technique scales well for multi-branch circuits.

6. Practical Tips for Engineers

1. **Keep Units Consistent**: Mixing volts, amperes, ohms, and milliamperes can lead to errors.
2. **Use SI Prefixes**: Convert kilovolts to volts (kV = 1,000 V) before plugging numbers into formulas.
3. **Leverage Software Tools**: MATLAB, LT-Spice, and Python libraries can validate hand calculations.

Downloaded from www.suitsbysuits.com by Elaina & Ellen • Explore the unseen. • Page 3 • 2026-06-28